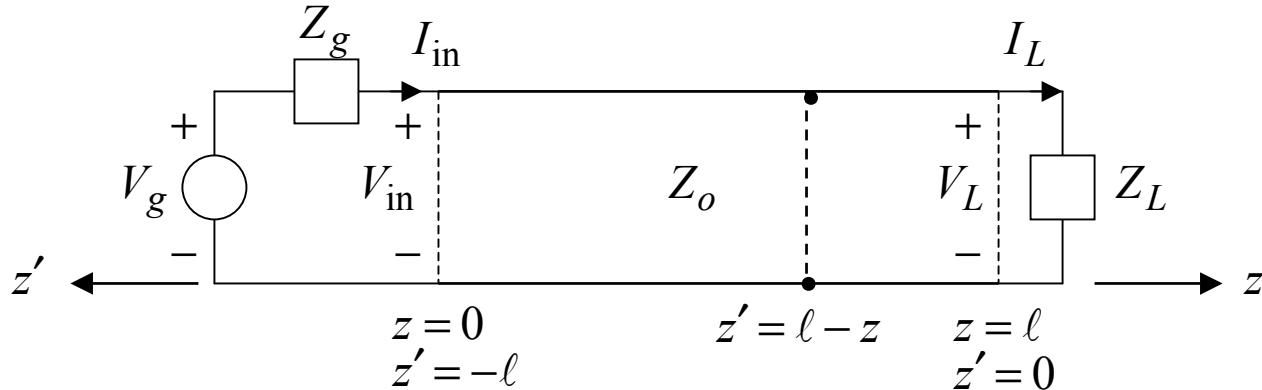


Exact voltage and current anywhere on a finite transmission line (D. K. Cheng)




Expressions for the exact phasor voltage and current:

$$V(z') = \underbrace{\frac{Z_o V_g}{Z_o + Z_g}}_{V_{in}} e^{-\gamma z} \left(\frac{1 + \Gamma_L e^{-2\gamma z'}}{1 - \Gamma_g \Gamma_L e^{-2\gamma \ell}} \right)$$

$$I(z') = \frac{V_g}{Z_o + Z_g} e^{-\gamma z} \left(\frac{1 - \Gamma_L e^{-2\gamma z'}}{1 - \Gamma_g \Gamma_L e^{-2\gamma \ell}} \right)$$


For a lossy line terminated with a load:

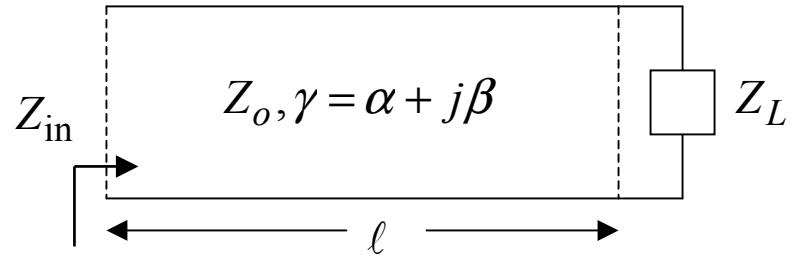

The input impedance is

$$Z_{in} = Z_o \left(\frac{Z_L + Z_o \tanh(\gamma \ell)}{Z_o + Z_L \tanh(\gamma \ell)} \right)$$




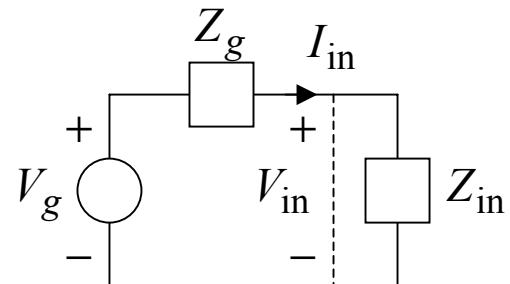
The equivalent circuit for computing the power into the line:



Matlab program
XlinePower.m

```
% compare numbers for input impedance
clear
zg=50; % generator impedance
z0=50; % characteristic impedance
zl=25+j*25; % load impedance
gg=(zg-z0)/(zg+z0); % generator reflection coefficient
gl=(zl-z0)/(zl+z0); % load reflection coefficient
% use 300 MHz so wave=lm and lengths will be in wavelengths
wave=3e8/1e8;
L=3.3; % length of line in wavelengths
b=2*pi/wave; % beta, phase constant
a=0.001; % alpha, attenuation constant
gam=a+j*b; % gamma
vg=1; % generator voltage
vm=z0*vg/(z0+zg);
% enter value of z (z=0 is the input; z=L is the load)
disp(' ')
disp(['z=0 is the input; z= ',num2str(L), ' is the load'])
%----- calculate power into the line (z=0) -----
z=0;
zp=L-z;
V=vm*exp(-gam*z)*(1+gl*exp(-2*gam*zp))/(1-gg*gl*exp(-2*gam*L));
I=vg/(z0+zg)*exp(-gam*z)*(1-gl*exp(-2*gam*zp))/(1-gg*gl*exp(-2*gam*L));
Pin=.5*real(V*conj(I));
disp(['power into the line using exact formulas: ',num2str(Pin)])
%----- calculate power to the load (z=L) -----
z=L;
zp=L-z;
V=vm*exp(-gam*z)*(1+gl*exp(-2*gam*zp))/(1-gg*gl*exp(-2*gam*L));
I=vg/(z0+zg)*exp(-gam*z)*(1-gl*exp(-2*gam*zp))/(1-gg*gl*exp(-2*gam*L));
PL=.5*real(V*conj(I));
disp(['power to the load using exact formulas: ',num2str(PL)])
% closed form
zin=z0*(zl+z0*tanh(gam*L))/(z0+zl*tanh(gam*L));
Vin=vg*zin/(zin+z0);
Iin=Vin/zin;
Pin=.5*real(Vin*conj(Iin));
disp(['power to the load using Vin and Iin: ',num2str(Pin)])
```

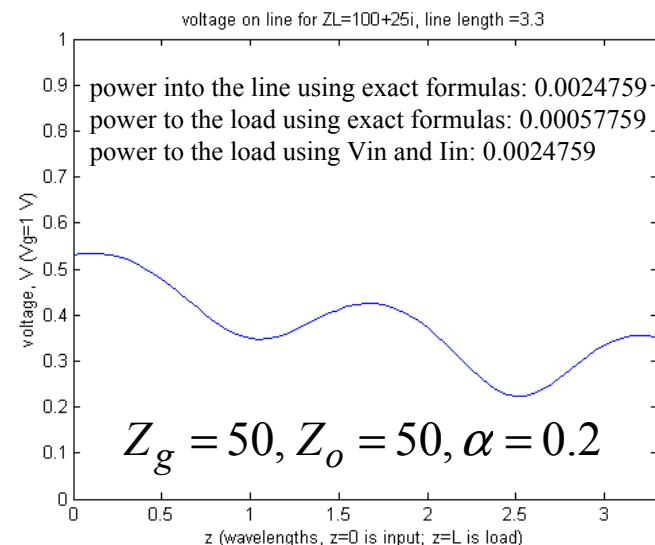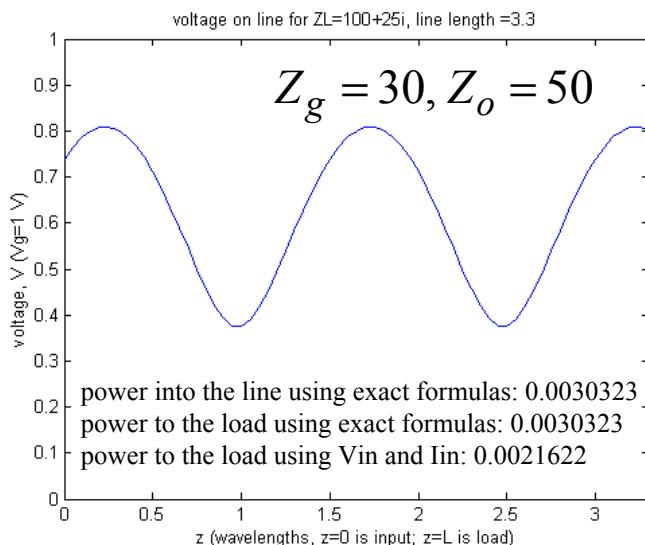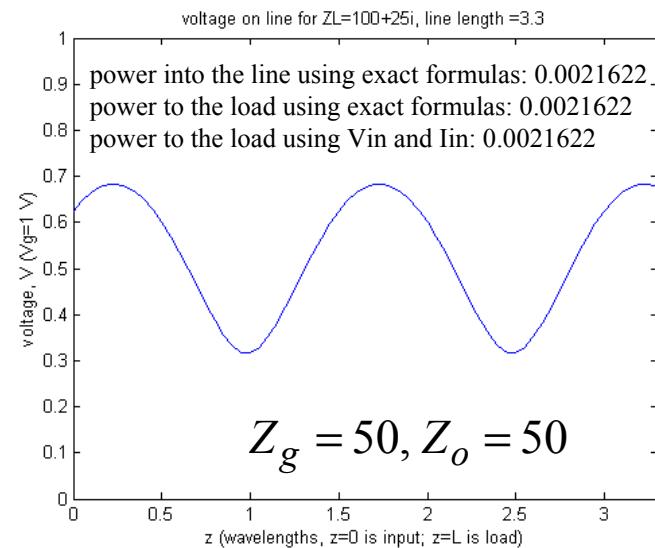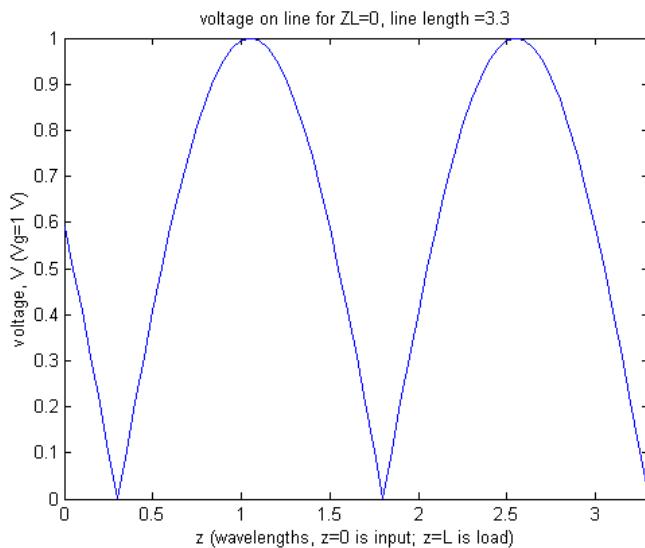For a lossless line, the power delivered to the load is the power into the line if $Z_g = Z_o$ (no reflections at the input end of the transmission line)



Reflections on a quarter wave transformer section

